

Proyecto Final - Circuitos Analogicos 2024-II

Gomez Gabriel, Gustavo Lozano

July 31, 2024

Full Adder - Truth Table

A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder Truth Table

Full Adder - Boolean Algebra

$$S = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

$$C_{out} = \overline{A}BC_{in} + A\overline{B}C_{in} + AB\overline{C}_{in} + ABC_{in}$$

Full Adder - Implementation

Takes 108 transistors.

$$S = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

Takes only 18 transistors (9 transistors by **XOR**).

$$S = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in} \quad (1)$$

$$= C_{in} [\overline{A}\overline{B} + AB] + \overline{A}\overline{B}\overline{C}_{in} + \overline{A}B\overline{C}_{in} \quad (2)$$

$$= C_{in} [(\overline{A} + B)(A + \overline{B})] + \overline{C}_{in}(\overline{A}\overline{B} + \overline{A}B) \quad (3)$$

$$= C_{in} [\overline{A}\overline{B}\overline{A}B] + \overline{C}_{in}(\overline{A}\overline{B} + \overline{A}B) \quad (4)$$

$$= C_{in}(\overline{A}\overline{B} + \overline{A}B) + \overline{C}_{in}(\overline{A}\overline{B} + \overline{A}B) \quad (5)$$

$$= C_{in} \oplus [\overline{A}\overline{B} + \overline{A}B] \quad (6)$$

$$= C_{in} \oplus (A \oplus B) \quad (7)$$

Full Adder - Implementation

Initial expression extracted from Truth Table.

$$C_{out} = \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in}$$

Reducer with *Karnaugh Map*[2].

$$C_{out} = AB + BC_{in} + AC_{in}$$

$$C_{out} = \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in} \quad (8)$$


$$= C_{in}(\bar{A}B + A\bar{B}) + AB(C_{in} + \bar{C}_{in}) \quad (9)$$

$$= C_{in}(\bar{A}B + A\bar{B}) + AB \quad (10)$$

$$= AB + C_{in}(A \oplus B) \quad (11)$$


In this expression we need 2 **AND** gate, 1 **OR** gate and 1 **XOR** (that we can **reuse** from *S* expression).**XOR**).

Full Adder - Logical Gates Circuit

 

A Full Adder Circuit

Two Bit Adder

 

MOSFET - Inversion Layer

 


Figure 3.7 The n-channel enhancement-mode MOSFET (a) with an applied gate voltage $v_{GS} < V_{TN}$, and (b) with an applied gate voltage $v_{GS} > V_{TN}$

MOSFET - Characteristic Curves

 


Figure 3.10 Family of i_D versus v_{DS} curves for an n-channel enhancement-mode MOSFET.

MOSFET - Equations

Table 3.1 Summary of the MOSFET current-voltage relationships

NMOS

Nonsaturation region ($v_{DS} < v_{DS}(\text{sat})$)

$$i_D = K_n[2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$$

Saturation region ($v_{DS} > v_{DS}(\text{sat})$)

$$i_D = K_n(v_{GS} - V_{TN})^2$$

Transition point

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

Enhancement mode

$$V_{TN} > 0$$

Depletion mode

$$V_{TN} < 0$$

PMOS

Nonsaturation region ($v_{SD} < v_{SD}(\text{sat})$)

$$i_D = K_p[2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$$

Saturation region ($v_{SD} > v_{SD}(\text{sat})$)

$$i_D = K_p(v_{SG} + V_{TP})^2$$

Transition point

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$




Enhancement mode

$$V_{TP} < 0$$

Depletion mode

$$V_{TP} > 0$$

Logic gates - MOSFET Inverter

  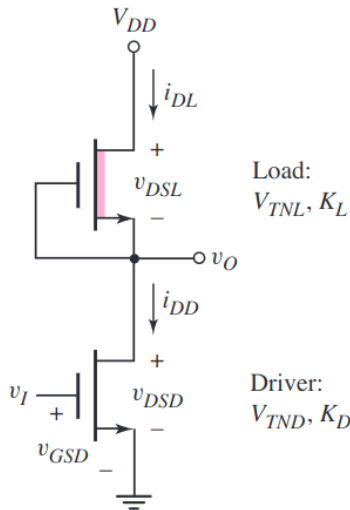

Logic gates - MOSFET Inverter - Transition Points

LOAD

$$v_{DSL} = V_{DD} - v_o = v_{GSL} - V_{TNL} = -V_{TNL}$$

Therefore, one transition point (LOAD) is at:

$$v_o = V_{DD} + V_{TNL}$$

DRIVER

$$v_{DSD} = v_o = V_{GSD} - V_{TND} = v_i - V_{TND}$$

Therefore, the other transition point (DRIVER) is at:

$$v_o = v_i - V_{TND}$$

Logic gates - MOSFET Inverter - Operation

- **load** nonsaturation and **driver** saturation (Q-point on A and B)

$$K_D[-V_{TND}]^2 = K_L[2(v_i - V_{TND})v_o - v_o^2]$$


- **load** and **driver** on saturation (Q-point on B and C)

$$K_D[v_i - V_{TND}]^2 = K_L[(V_{DD} - v_o) - V_{TNL}]^2$$


- **load** saturation and **driver** nonsaturation (Q-point on C and D)

$$K_D[v_i - V_{TND}]^2 = K_L[2(-V_{TND})(V_{DD} - v_o) - (V_{DD} - v_o)^2]$$

Logic gates - MOSFETS - Inverter

 

Logic gates - MOSFETS - NOR

 

**Tabla de
verdad**

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

Logic gates - MOSFETS - NAND

 


Tabla de verdad

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

Logic gates - MOSFETS - XOR


 


Tabla de verdad

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

Logic gates - MOSFETS - AND and OR

 

Inversor

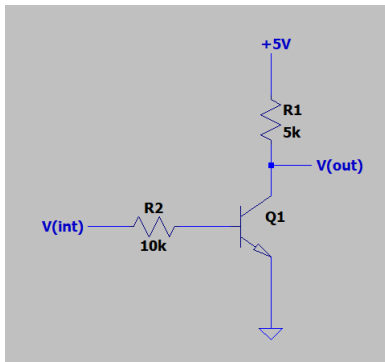


Tabla de verdad

A	\overline{A}
0	1
1	0

Puerto OR

Circuito OR


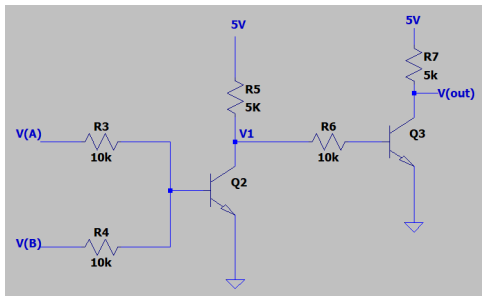


Tabla de verdad

A	B	$A + B$
0	0	0
1	0	1
0	1	1
1	1	1

Puerto AND

Circuito NAND

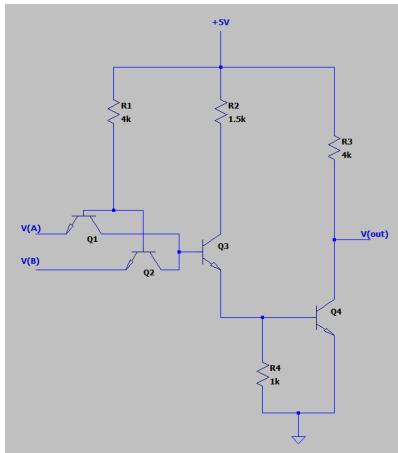

Circuito equivalente del AND


 


Tabla de verdad

A	B	$A \cdot B$
0	0	0
1	0	0
0	1	0
1	1	1

Puerto XOR

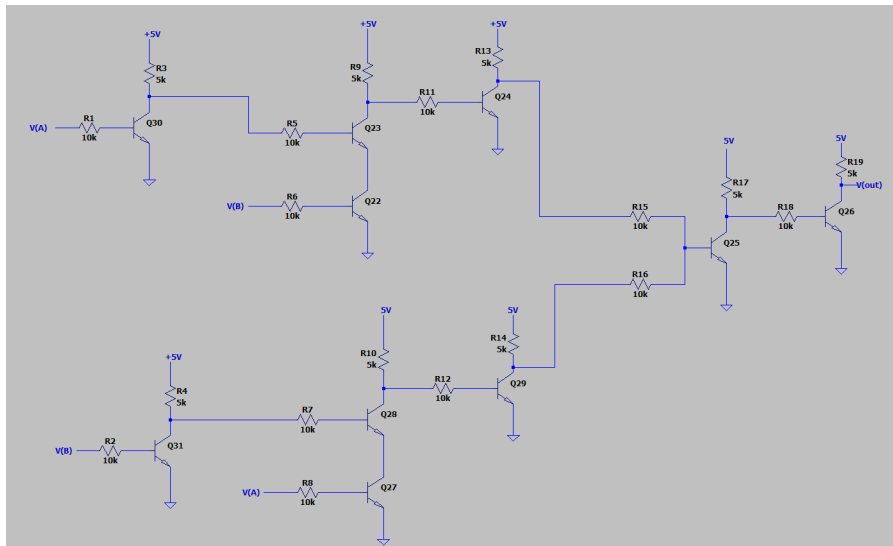

Puerto XOR

Tabla de verdad

A	B	$A \oplus B$
0	0	0
1	0	1
0	1	1
1	1	0

Observaciones

- Al utilizar interruptores de un solo sentido en cada pin de entrada, si el interruptor estaba abierto, el voltaje obtenia cualquier valor. Esto se corrigió usando de dos vías, esto permitía definir correctamente el 0 y 1.
- Dado que no se pudo obtener un n-channel depletion mode, se reemplazó por una resistencia de menor valor posible para no afectar el 1 lógico; y evitar dañar la fuente de alimentación.

Conclusiones

- Ambos *Full adder* presentaron un correcto funcionamiento, se creó 2 *bits adder* usando MOSFET y BJT.

References

Images and circuits were extracted from [3][4][1].



Robert L Boylestad, Louis Nashelsky, Carlos Mendoza Barraza, and Agustín Suárez Fernández.

Electrónica: teoría de circuitos y dispositivos electrónicos, volume 8. PEARSON educación, 2018.



Thomas L Floyd.

Digital Fundamentals, by Pearson. Pearson Education India, 2015.



Yusuf Leblebici and Sung-Mo Kang.

CMOS digital integrated circuits: analysis and design. McGraw-Hill New York, 1996.



Donald A Neamen.

Microelectronics: circuit analysis and design, volume 43. McGraw-Hill New York, 2007.